

In-Class Assignment

PHY 2105 (A)

Assignment IV

Please rename your file with InClassAssignIV_ID before uploading via lms.

1. To have maximum use of electrical power what combination of four bulbs should you use? Justify your answer.
2. For the circuit below, calculate the current drawn from the battery and the current in the 6Ω resistor.

