

In-Class Assignment

PHY 2105 (A)

Assignment II

Please rename your file with InClassAssignII_ID before uploading via lms.

1. Justify that the motion of the LRC circuit can be converted to that of a simple harmonic oscillator with certain changes in its components.
2. Sketch the Lissajous' figure for the inputs of $v = C\cos(\omega t + \pi/4)$ and $v' = D\cos(\omega t + \pi/2)$, which are perpendicular to each other.
3. In oscillatory circuit $L = 0.4\text{H}$, $C = 0.0020\mu\text{F}$. What is maximum value of resistance(R) for the circuit to be oscillatory?