
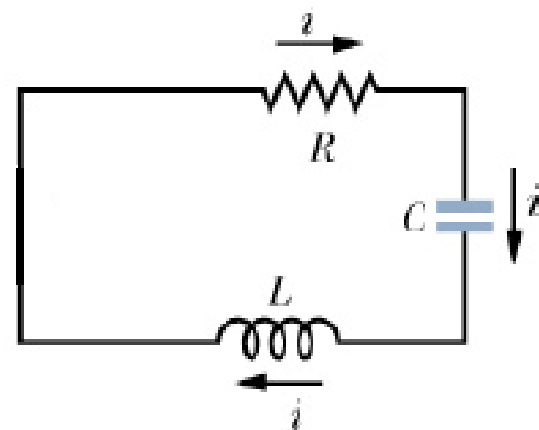


RLC circuit

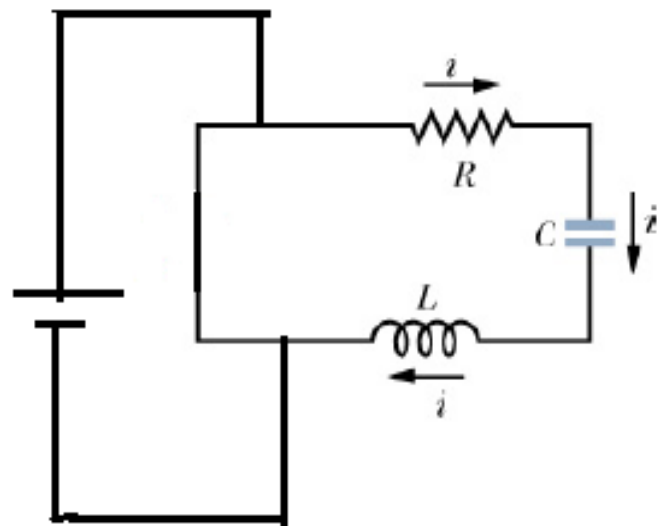

- Voltage across resistor R

$$V_R = iR$$

- Voltage across capacitor C

$$V_C = \frac{Q}{C}$$

- Voltage across inductor L

$$V_L = L \frac{di}{dt}$$

- According to

Kirchhoff's voltage law

$$iR + \frac{Q}{C} + L \frac{di}{dt} = 0$$

Rewrite the equation

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

Comparing with the equation

$$\frac{d^2 x}{dt^2} + \gamma \frac{dx}{dt} + \omega_0^2 x = 0$$

Where

$$\gamma = \frac{R}{L} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

Three distinguish cases are

i) $\frac{1}{LC} > \frac{R^2}{4L^2}$ Oscillatory behavior

ii) $\frac{1}{LC} = \frac{R^2}{4L^2}$ Critical damping

iii) $\frac{1}{LC} < \frac{R^2}{4L^2}$ Over damping

Case i) $\frac{1}{LC} > \frac{R^2}{4L^2}$

Solution of the differential equation

$$Q(t) = Ae^{-\frac{R}{2L}t} \cos(\omega_1 t + \phi)$$

Where in damping,

Angular Frequency of oscillation, $\omega_1 = \sqrt{\left(\frac{1}{LC} - \frac{R^2}{4L^2}\right)}$

Frequency of oscillation,

$$f = \frac{1}{2\pi} \sqrt{\left(\frac{1}{LC} - \frac{R^2}{4L^2}\right)}$$

When resonance occurs, the driven frequency ω_d from an external emf source is equal to the natural frequency ω_0 .

$$\omega_d = \omega_0 = \frac{1}{\sqrt{LC}} \quad (\text{resonance}).$$


Simply we can calculate,

Angular Resonant Frequency,

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

Linear Resonant Frequency,
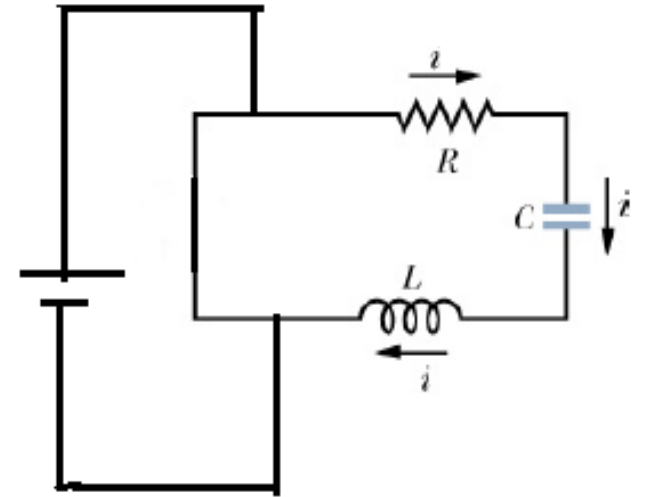
$$f_0 = \frac{1}{2\pi} \sqrt{\left(\frac{1}{LC}\right)}$$



Here both of them are Resonant Frequency, if you are trying to calculate Linear resonant frequency you will calculate f_0 and if you want to calculate resonant angular frequency you will calculate ω_0